

# R5432V Temperature Protection Circuit Example



Reported : 台北工程學部


Date : Jan. 16<sup>th</sup> 2020



# Circuit Example for 5 Cell Protection

**AENEAS**

Whole circuit of temperature protection

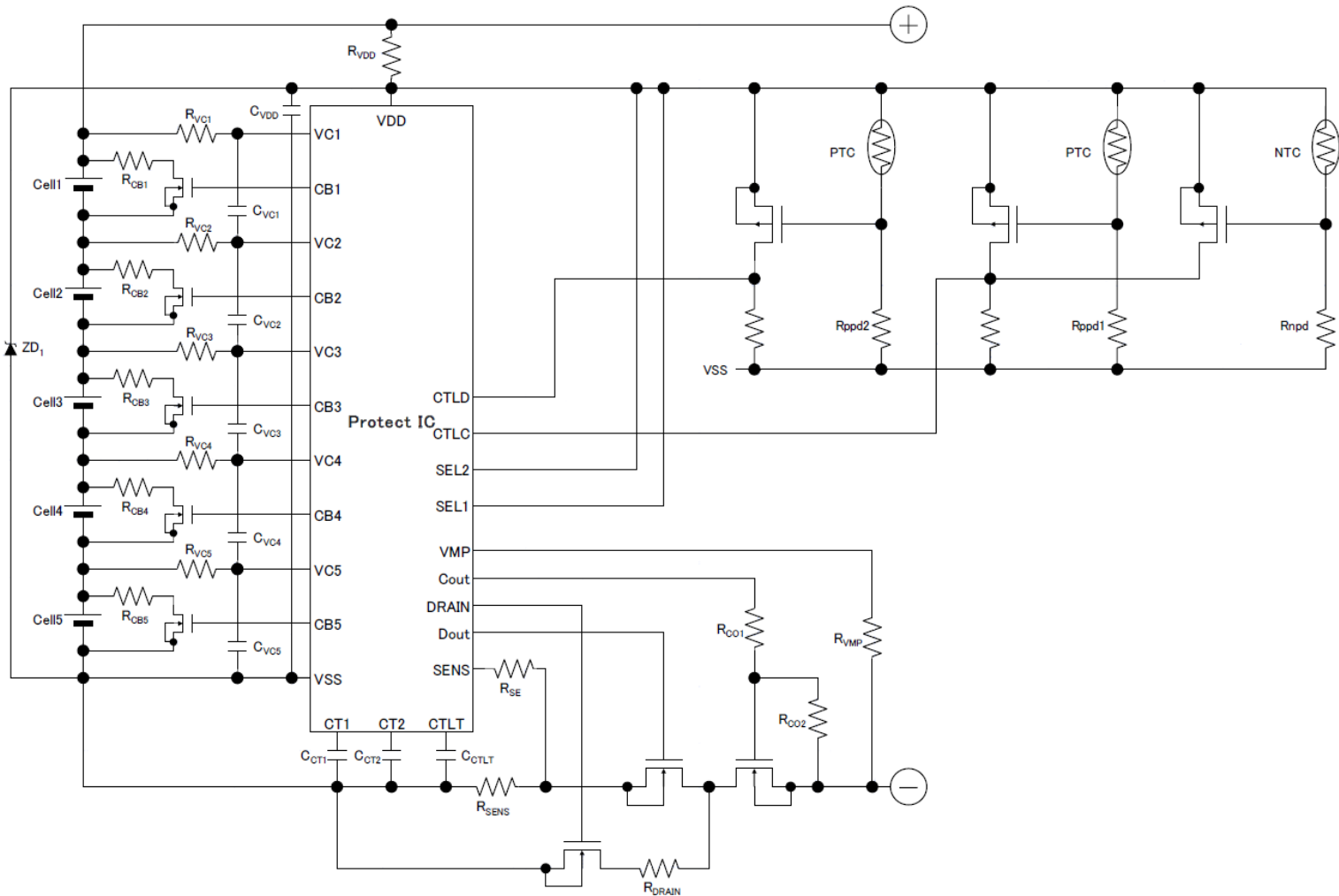




# Circuit Example for 5 Cell Protection


**AENEAS**

Partial circuit of temperature protection

## High Temperature Protection

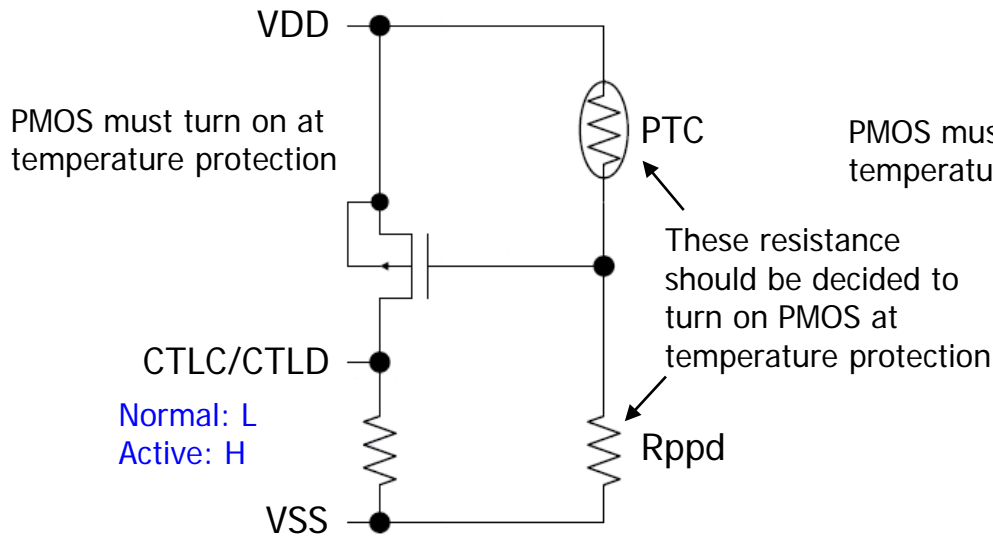

## Low Temperature Protection

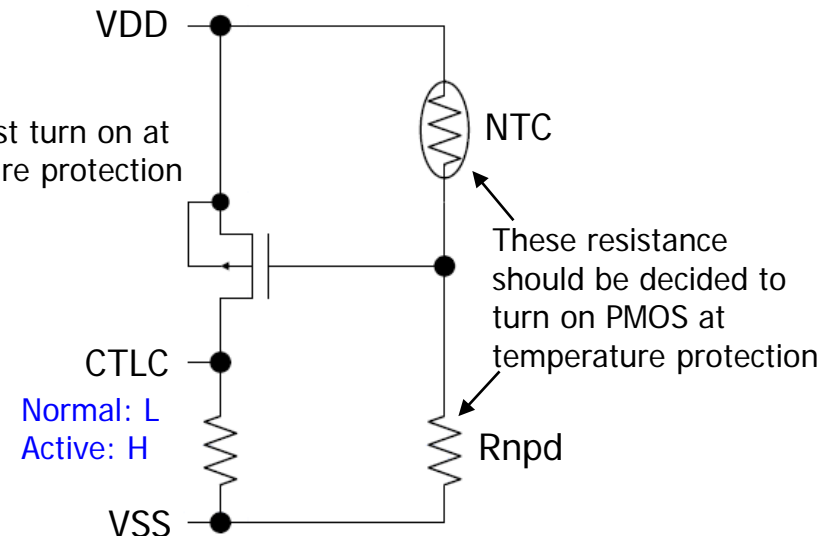

**COUT(DOUT) turns off when CTLC(CTLD) is inputted VDD voltage**



With temperature protection

## Technical Note 1

High temperature protection

PMOS Gate connect to between PTC and resistor, and CTLC/CTLD connect to between PMOS drain and resistor.

The value of Rptc and Rppd should be decided to turn on PMOS at temperature protection.

Ex:

Rptc : PTC resistance at temperature protection

Rppd : Rppd resistance

Vthpp : Threshold voltage of PMOS

Vctl: Input voltage of CTLC/CTLD

If  $VDD * \{ Rppd / (Rppd + Rptc) - 1 \}$  becomes less than Vthpp, then PMOS turns on and CTLC/CTLD is inputted VDD voltage.

It is important for this circuit to select PMOS, PTC and Rppd properly.



With temperature protection

## Technical Note 1

Low temperature protection

PMOS Gate connect to between NTC and resistor, and CTLC connect to between PMOS drain and resistor.

The value of Rntc and Rnpd should be decided to turn on PMOS at temperature protection.

Ex:

Rntc : NTC resistance at temperature protection

Rnpd : Rnpd resistance

Vthpn : Threshold voltage of PMOS

Vctl: Input voltage of CTLC

If  $VDD * \{ Rnpd / (Rnpd + Rntc) - 1 \}$  becomes less than Vthpn, then PMOS turns on and CTLC is inputted VDD voltage.

It is important for this circuit to select PMOS, NTC and Rnpd properly.



*Thank You!*

